

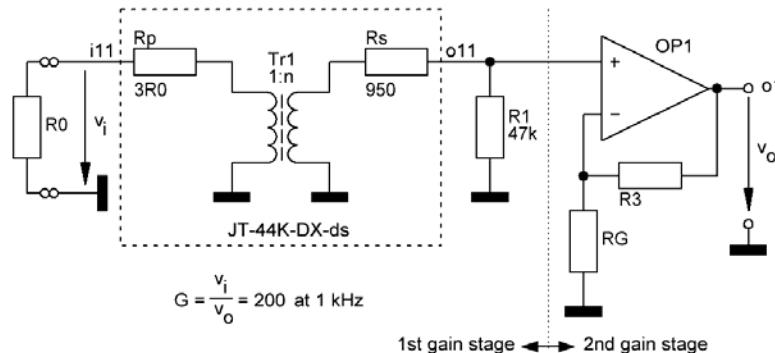
Amp with unbalanced step-up transformer: SN and gain calculations

Fig. 1 Amp with warm transformer and data of JT-44K-DX-ds' datasheet & OP37G

<u>Subscripts :</u>	$20k = 20\text{Hz} \dots 20\text{kHz}$	$o1 = \text{output } 1$	$1 = 1 \text{ Hz eg } B_1 \text{ or } = \text{simple numbering}$
$\text{amp} = \text{warm Fig. 1}$	$\text{cld} = \text{cold}$	$\text{ds} = \text{datasheet}$	$i, o = \text{i/p, o/ referred}$
$e = \text{dB with } 20\log(\dots)$	$m = \text{measured}$	$n = \text{noise density in } \sqrt{\text{Hz}}$	
$N = \text{rms noise voltage in } B_{20k}$	$s = \text{simulated}$	$\text{tot} = \text{total}$	$\text{wrn} = \text{warm}$

$$T := 300.15\text{K} \quad k := 1.38065 \cdot 10^{-23} \text{V}\cdot\text{A}\cdot\text{s}\cdot\text{K}^{-1} \quad B_1 := 1\text{Hz} \quad \text{TOL} := 10^{-18}$$

$$f := 10\text{Hz}, 15\text{Hz}..100\text{kHz} \quad h := 1\text{kHz} \quad B_{20k} := 19980\text{Hz} \quad v_{i,\text{nom}} := 0.5 \cdot 10^{-3}\text{V} \quad v_{o,\text{nom}} := 1\text{V}$$

0. Relevant transformer data :

$$\begin{aligned} R_p &:= 3.0\Omega & R_s &:= 950\Omega & R_0 &:= 0\Omega, 0.5\Omega .. 40\Omega & R_i &:= 47 \cdot 10^3 \Omega \\ L_p &:= 1.3\text{H} & L_s &:= 130\text{H} & & & n := \sqrt{\frac{L_s}{L_p}} \\ &&&&&& n = 10.000 \end{aligned}$$

1. First gain stage: calculated noise of the warm trafo network at room temperature :

$$Z_{in} := \frac{R_s + R_i}{n^2} \quad Z_{in} = 479.500 \Omega$$

$$Z_{in,tot} := R_p + \frac{R_s + R_i}{n^2} \quad Z_{in,tot} = 482.500 \Omega$$

$$Z_{out,tot}(R_0) := R_s + n^2 \cdot (R_0 + R_p) \quad Z_{out,tot}(0\Omega) = 1250.000 \Omega$$

$$G_p(R_0) := \frac{Z_{in}}{R_0 + Z_{in,tot}} \quad G_p(0\Omega) = 0.994$$

$$G_s := \frac{R_i}{R_s + R_i} \quad G_s = 0.980$$

$$G_1(R_0) := G_s \cdot G_p(R_0) \cdot n \quad G_{1st} := G_1(0\Omega) \quad G_{1st} = 9.740933$$

$$e_{N.o11.wrm}(R0) := \sqrt{4 \cdot k \cdot T \cdot B_{20k} \left[(R0 + Rp) \cdot G1(R0)^2 \dots + Rs \cdot \left(\frac{Ri}{Z_{out,tot}(R0) + Ri} \right)^2 + Ri \cdot \left(\frac{Z_{out,tot}(R0)}{Z_{out,tot}(R0) + Ri} \right)^2 \right]} \quad (1)$$

$$e_{N.o11.wrm}(0\Omega) = 635.030 \times 10^{-9} \text{ V}$$

Simulation result with $R0 = 0\Omega \Rightarrow e_{N.o11.wrm.s} := 635.030 \cdot 10^{-9} \text{ V}$

$$D_{e.wrm}(R0) := 20 \cdot \log \left(\frac{e_{N.o11.wrm}(R0)}{e_{N.o11.wrm.s}} \right) \quad D_{e.wrm}(0\Omega) = -0.000 \quad [\text{dB}]$$

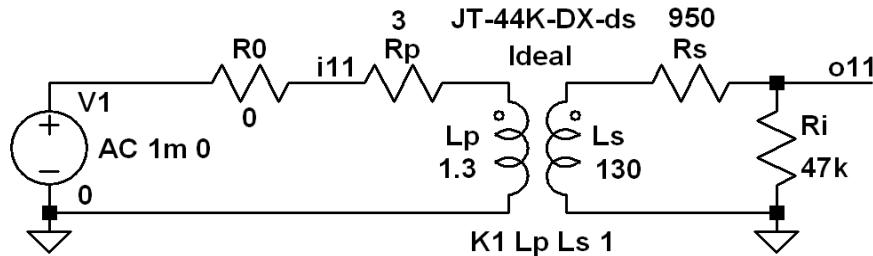


Fig. 2
Simulation schematic of
the input network with
warm JT-44K-DX-ds
transformer

2. First gain stage: calculated noise of the trafo network at room temperature,
however, with a noiseless = cold transformer :

$$\Rightarrow e_{N.o11.cld}(R0) := \sqrt{4 \cdot k \cdot T \cdot B_{20k} \left[R0 \cdot G1(R0)^2 + Ri \cdot \left(\frac{Z_{out,tot}(R0)}{Z_{out,tot}(R0) + Ri} \right)^2 \right]} \quad (2)$$

$$e_{N.o11.cld}(0\Omega) = 102.212 \times 10^{-9} \text{ V}$$

Simulation result with $R0 = 0\Omega \Rightarrow e_{N.o11.cld.s} := 102.212 \cdot 10^{-9} \text{ V}$

$$D_{e.cld}(R0) := 20 \cdot \log \left(\frac{e_{N.o11.cld}(R0)}{e_{N.o11.cld.s}} \right) \quad D_{e.cld}(0\Omega) = -0.000 \quad [\text{dB}]$$

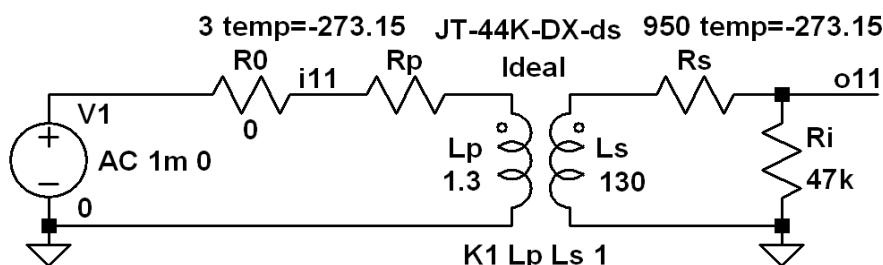


Fig. 3
Simulation schematic of
the input network with
cold JT-44K-DX-ds
transformer

3. First gain stage: deltas between the warm and cold situation = Worsening effect W of the cold transformer vs. the warm one :

$$W_{e,o}(R_0) := 20 \cdot \log \left(\frac{e_{N.o11.cld}(R_0)}{e_{N.o11.wrm}(R_0)} \right) \quad W_{e,o}(0\Omega) = -15.866 \text{ [dB]} \quad (3)$$

$$W_{e,s} := 20 \cdot \log \left(\frac{e_{N.o11.cld.s}}{e_{N.o11.wrm.s}} \right) \quad W_{e,s} = -15.866 \text{ [dB]}$$

$$W_{e,s.10} := -3.281 \text{ [dB]}$$

$$W_{e,o}(0\Omega) - W_{e,s} = -0.000 \text{ [dB]}$$

$$W_{e,o}(10\Omega) - W_{e,s.10} = 0.000 \text{ [dB]}$$

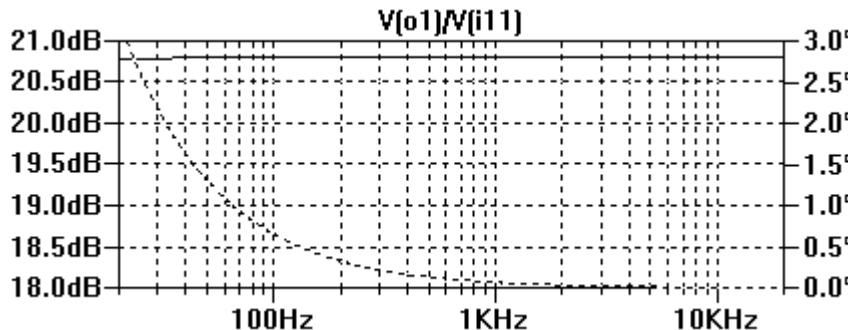


Fig. 4
F (solid) & P
(dotted)
responses of
Figs. 2 & 3

4. First gain stage: graphs :

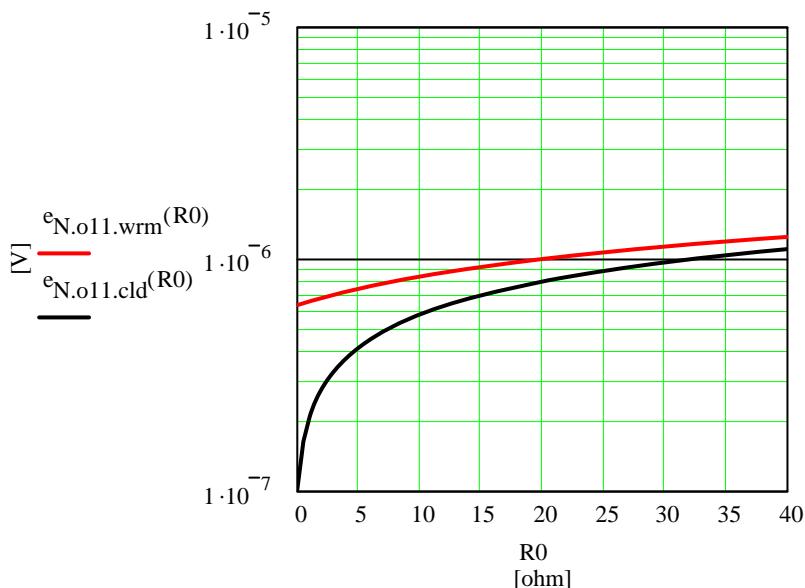


Fig. 5
R0-dependent warm
(red) and cold (blk)
rms output noise
voltages, (1) & (2)

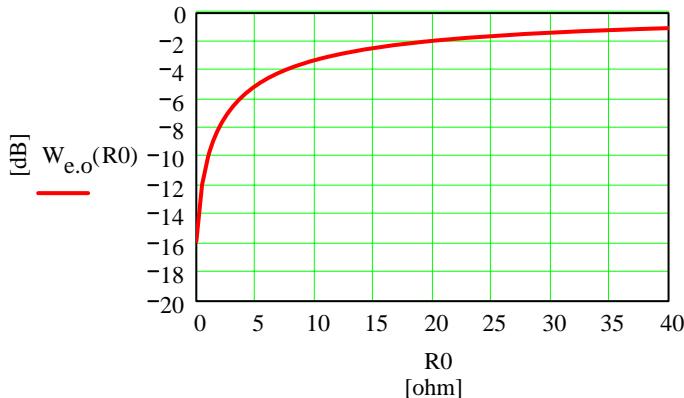


Fig. 6
Trace of equ. (3):
Worsening of the
cold transformer
vs. R0

5. Second gain stage: gain and component data as of Fig. 1 :

$$R1 := 47 \cdot 10^3 \Omega$$

$$R1 = Ri$$

$$R3 := 1 \cdot 10^3 \Omega$$

$$G_{\text{tot}} := 200$$

$$G_{2\text{nd}} := \frac{G_{\text{tot}}}{G_{1\text{st}}}$$

$$G_{2\text{nd}} = 20.532$$

$$G_{2\text{nd}} = 1 + \frac{R3}{RG}$$

$$RG := \frac{R3}{G_{2\text{nd}} - 1}$$

$$RG = 51.198 \Omega$$

6. Amp complete: calculation of the noise voltages :

Note: OP27 & OP37 have 100% correlated input referred current noise sources !
Voltage & current noise data taken from AD's datasheet

6.1 Relevant resistance data from the 1st gain stage :

$$Z_{i,\text{tot}}(R0) := \frac{Z_{\text{out,tot}}(R0) \cdot R1}{Z_{\text{out,tot}}(R0) + R1}$$

$$Z_{i,\text{tot}}(0\Omega) = 1.218 \times 10^3 \Omega$$

6.2 Relevant noise data of the op-amps :

$$e_{n,i1} := 3.2 \cdot 10^{-9} V \quad f_{c,e1} := 2.7 \text{Hz} \quad i_{n,i1} := 0.4 \cdot 10^{-12} A \quad f_{c,i1} := 120 \text{Hz}$$

$$e_{n,i1}(f) := e_{n,i1} \cdot \sqrt{\left(\frac{f}{f_{c,e1}}\right)^{-1} + 1}$$

$$i_{n,i1}(f) := i_{n,i1} \cdot \sqrt{\left(\frac{f}{f_{c,i1}}\right)^{-1} + 1}$$

6.3 Relevant resistance data and corresponding noise :

$$R_f := \frac{RG \cdot R_3}{RG + R_3}$$

$$R_f = 48.705 \Omega$$

$$e_{n,Rf} := \sqrt{4 \cdot k \cdot T \cdot B_1 \cdot R_f}$$

$$e_{n,Rf} = 898.517 \times 10^{-12} V$$

6.4 Noise voltage at the output of the warm Amp :

$$e_{n,o11.wrm}(R_0) := e_{N,o11.wrm}(R_0) \cdot \sqrt{\frac{B_1}{B_{20k}}}$$

$$e_{n,o11.wrm}(0\Omega) = 4.493 \times 10^{-9} V$$

Plus correlated current noise of the op-amps taken into account :

$$e_{n,o.wrm}(f, R_0) := G_{2nd} \cdot \sqrt{e_{n,i1}(f)^2 + e_{n,Rf}^2 + i_{n,i1}(f)^2 \cdot (R_f + Z_{i,tot}(R_0))^2 + e_{n,o11.wrm}(R_0)^2} \quad (4)$$

$$e_{n,o.wrm}(h, 0\Omega) = 115.319 \times 10^{-9} V$$

$$e_{n,i.wrm}(f, R_0) := \frac{e_{n,o.wrm}(f, R_0)}{G_{tot}}$$

$$e_{n,i.wrm}(h, 0\Omega) = 576.593 \times 10^{-12} V \quad (5)$$

$$e_{N,i.wrm}(R_0) := \sqrt{\frac{1}{B_1} \cdot \int_{20Hz}^{20000Hz} (|e_{n,i.wrm}(f, R_0)|)^2 df}$$

$$e_{N,i.wrm}(0\Omega) = 81.452 \times 10^{-9} V$$

$$e_{N,o.wrm}(R_0) := \sqrt{\frac{1}{B_1} \cdot \int_{20Hz}^{20000Hz} (|e_{n,o.wrm}(f, R_0)|)^2 df}$$

$$e_{N,o.wrm}(0\Omega) = 16.290 \times 10^{-6} V$$

$$SN_{o.wrm}(R_0) := 20 \cdot \log \left(\frac{e_{N,o.wrm}(R_0)}{v_{o,nom}} \right)$$

$$SN_{o.wrm}(0\Omega) = -95.761 \text{ [dBV]}$$

Simulation result with $R_0 = 0\Omega \Rightarrow SN_{o.wrm,s} := -95.761 \text{ [dBV]}$

$$SN_{o.wrm}(0\Omega) - SN_{o.wrm,s} = -0.000 \text{ [dB]}$$

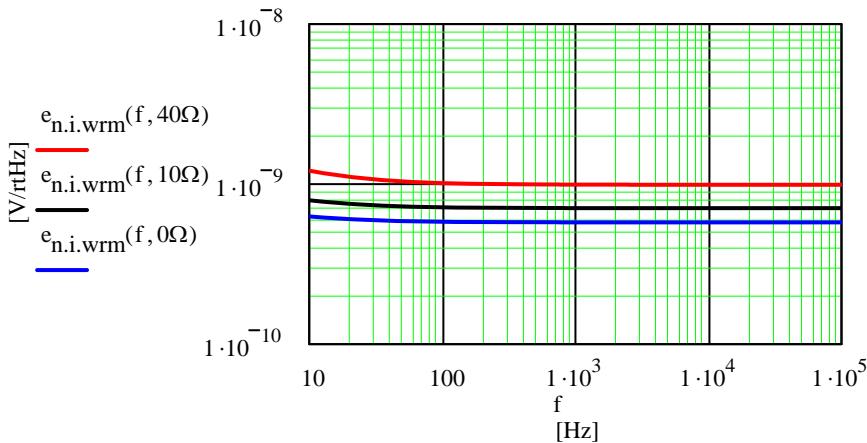


Fig. 7
Amp's
R0-dependent
input noise voltage
densities vs.
frequency for R0 =
0Ω, 10Ω, and 40Ω
à la equ. (4)

7. Calculation: Amp's input and output referred noise voltage densities and SNs - cold version of JT-44K-DX-ds :

$$e_{n.Rs} := \sqrt{4 \cdot k \cdot T \cdot B_1 \cdot R_s} \quad e_{n.Rs} = 3.968 \times 10^{-9} \text{ V}$$

$$R_{p.sec} := n^2 \cdot R_p \quad R_{p.sec} = 300.000 \Omega$$

$$e_{n.Rp.sec} := \sqrt{4 \cdot k \cdot T \cdot B_1 \cdot R_{p.sec}} \quad e_{n.Rp.sec} = 2.230 \times 10^{-9} \text{ V}$$

$$e_{n.o.cld}(f, R_0) := \sqrt{e_{n.o.wrm}(f, R_0)^2 - (e_{n.Rs}^2 + e_{n.Rp.sec}^2) \cdot G_{2nd}^2 \cdot G_s^2 \cdot G_p(R_0)^2} \quad (6)$$

$$e_{n.o.cld}(h, 0\Omega) = 70.784 \times 10^{-9} \text{ V}$$

$$e_{n.i.cld}(f, R_0) := e_{n.o.cld}(f, R_0) \cdot G_{tot}^{-1} \quad e_{n.i.cld}(h, 0\Omega) = 353.918 \times 10^{-12} \text{ V} \quad (7)$$

$$e_{N.o.cld}(R_0) := \sqrt{\frac{1}{B_1} \cdot \int_{20Hz}^{20000Hz} (|e_{n.o.cld}(f, R_0)|)^2 df} \quad e_{N.o.cld}(0\Omega) = 9.989 \times 10^{-6} \text{ V}$$

$$e_{N.i.cld}(R_0) := \sqrt{\frac{1}{B_1} \cdot \int_{20Hz}^{20000Hz} (|e_{n.i.cld}(f, R_0)|)^2 df} \quad e_{N.i.cld}(0\Omega) = 49.946 \times 10^{-9} \text{ V}$$

$$SN_{i.cld}(R_0) := 20 \cdot \log \left(\frac{e_{N.i.cld}(R_0)}{v_{i.nom}} \right) \quad SN_{i.cld}(0\Omega) = -80.009 \quad [\text{dB}]$$

$$SN_{o.cld}(R_0) := 20 \cdot \log \left(\frac{e_{N.o.cld}(R_0)}{v_{o.nom}} \right) \quad SN_{o.cld}(0\Omega) = -100.009 \quad [\text{dBV}]$$

Simulation result with R0 = 0Ω => $SN_{o.cld.s} := -100.009$ [dBV]

$$SN_{o.cld}(0\Omega) - SN_{o.cld.s} = -0.000 \quad [\text{dB}]$$

8. Amp's 2nd gain stage with input shorted to ground:

output referred noise voltage densities and SNs : $R_s := 0\Omega$ $R_p := 0\Omega$ $R_1 := 0\Omega$

$$e_{n.o.2nd}(f) := G_{2nd} \cdot \sqrt{e_{n.i1}(f)^2 + e_{n.Rf}^2 + i_{n.i1}(f)^2 \cdot R_f^2} \quad e_{n.o.2nd}(h) = 68.330 \times 10^{-9} \text{ V}$$

$$e_{N.o.2nd} := \sqrt{\frac{1}{B_1} \cdot \int_{20\text{Hz}}^{20000\text{Hz}} (|e_{n.o.2nd}(f)|)^2 df} \quad e_{N.o.2nd} = 9.651 \times 10^{-6} \text{ V}$$

$$SN_{o.2nd} := 20 \cdot \log \left(\frac{e_{N.o.2nd}}{v_{o.nom}} \right) \quad SN_{o.2nd} = -100.309 \quad [\text{dBV}]$$

Simulation result with $R_0 = 0\Omega \Rightarrow SN_{o.2nd,s} := -100.309 \quad [\text{dBV}]$

$$SN_{o.2nd} - SN_{o.2nd,s} = 0.000 \quad [\text{dB}]$$

9. Current noise impact CNI at $R_0 = 0\Omega$:

$$CNI := SN_{o.cld}(0\Omega) - SN_{o.2nd} \quad CNI = 0.300 \quad [\text{dB}]$$

10. Amp graphs :

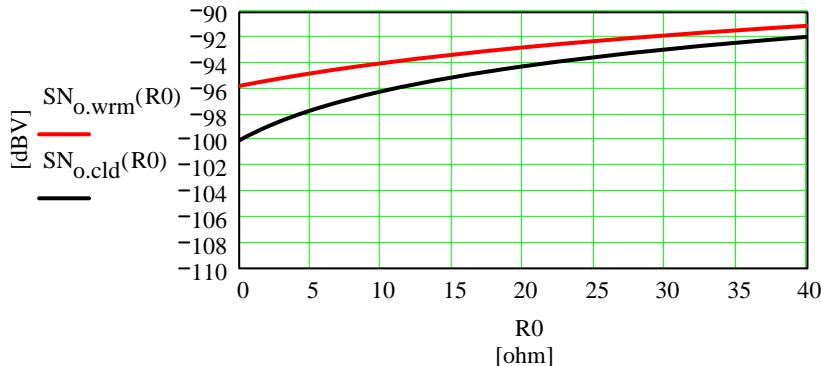


Fig. 8
Traces of the
 R_0 -dependent SNs of
the warm Amp vs. the
cold one, derived from
equ. (4) & (6)

Worsening W of the output referred SN of the warm Amp versus the cold one :

$$W_o(R_0) := SN_{o.cld}(R_0) - SN_{o.wrm}(R_0) \quad W_o(10\Omega) = -2.202 \quad [\text{dB}] \quad (8)$$

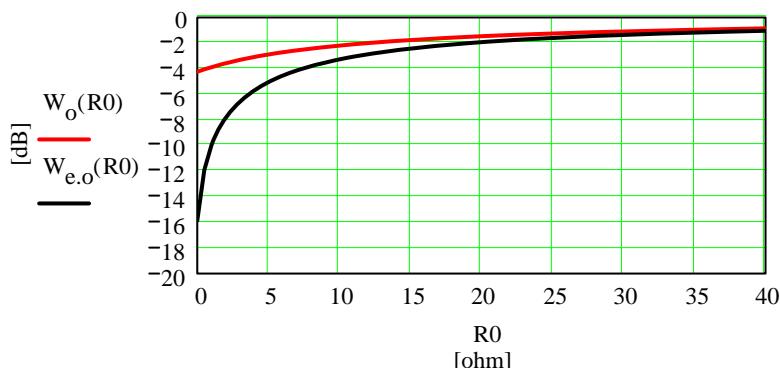


Fig. 9
Trace of the
 R_0 -dependent SN
worsening W of the cold
Amp vs. the warm one,
equ. (8) (red) plus trace
of Fig. 6 trafo alone equ.
(3) (blk)

11. Input referred RIAA equalized & A-weighted SNs :

$$A(f) := \frac{1.259}{1 + \left(\frac{20.6\text{Hz}}{f}\right)^2} \cdot \frac{1}{\sqrt{1 + \left(\frac{107.7\text{Hz}}{f}\right)^2}} \cdot \frac{1}{\sqrt{1 + \left(\frac{737.9\text{Hz}}{f}\right)^2}} \cdot \frac{1}{1 + \left(\frac{f}{12200\text{Hz}}\right)^2}$$

$$R_{1\text{kHz}} := \frac{\sqrt{1 + \left(2 \cdot \pi \cdot 1\text{kHz} \cdot 318 \cdot 10^{-6} \text{s}\right)^2}}{\sqrt{1 + \left(2 \cdot \pi \cdot 1\text{kHz} \cdot 3180 \cdot 10^{-6} \text{s}\right)^2} \cdot \sqrt{1 + \left(2 \cdot \pi \cdot 1\text{kHz} \cdot 75 \cdot 10^{-6} \text{s}\right)^2}} \quad R_{1\text{kHz}} = 101.030 \times 10^{-3}$$

$$R(f) := \frac{\sqrt{1 + \left(2 \cdot \pi \cdot f \cdot 318 \cdot 10^{-6} \text{s}\right)^2}}{\sqrt{1 + \left(2 \cdot \pi \cdot f \cdot 3180 \cdot 10^{-6} \text{s}\right)^2} \cdot \sqrt{1 + \left(2 \cdot \pi \cdot f \cdot 75 \cdot 10^{-6} \text{s}\right)^2}} \cdot (R_{1\text{kHz}})^{-1} \quad R(1\text{kHz}) = 1.000$$

$$SN_{\text{wrn.ariaa.i}}(R_0) := 20 \cdot \log \left[\frac{\sqrt{\frac{1}{B_1} \int_{20\text{Hz}}^{20000\text{Hz}} (|e_{\text{n.i.wrn}}(f, R_0)|)^2 \cdot (|A(f)|)^2 \cdot (|R(f)|)^2 df}}{v_{i,\text{nom}}} \right] \quad (9)$$

$$SN_{\text{cld.ariaa.i}}(R_0) := 20 \cdot \log \left[\frac{\sqrt{\frac{1}{B_1} \int_{20\text{Hz}}^{20000\text{Hz}} (|e_{\text{n.i.cld}}(f, R_0)|)^2 \cdot (|A(f)|)^2 \cdot (|R(f)|)^2 df}}{v_{i,\text{nom}}} \right] \quad (10)$$

Simulation result with $R_0 = 0\Omega \Rightarrow SN_{\text{wrn.ariaa.i.s.0}} := -83.692 \quad SN_{\text{wrn.ariaa.i}}(0\Omega) = -83.692 \text{ [dB(A)]}$

Simulation result with $R_0 = 10\Omega \Rightarrow SN_{\text{wrn.ariaa.i.s.10}} := -81.911 \quad SN_{\text{wrn.ariaa.i}}(10\Omega) = -81.912 \text{ [dB(A)]}$

Simulation result with $R_0 = 40\Omega \Rightarrow SN_{\text{wrn.ariaa.i.s.40}} := -78.976 \quad SN_{\text{wrn.ariaa.i}}(40\Omega) = -78.978 \text{ [dB(A)]}$

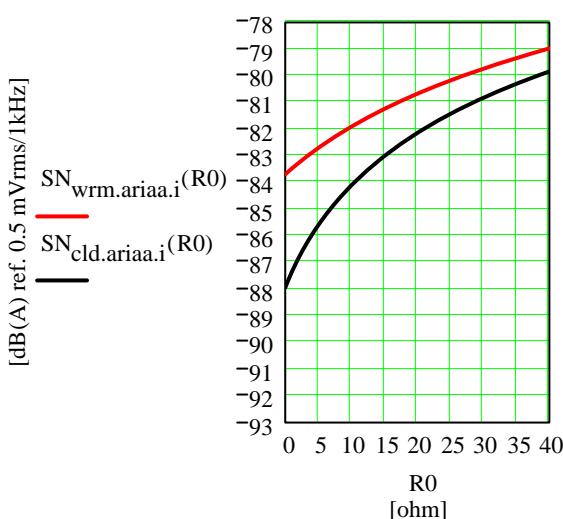


Fig. 10
Traces of the
R0-dependent input
referred warm &
cold SNs. (9) & (10)

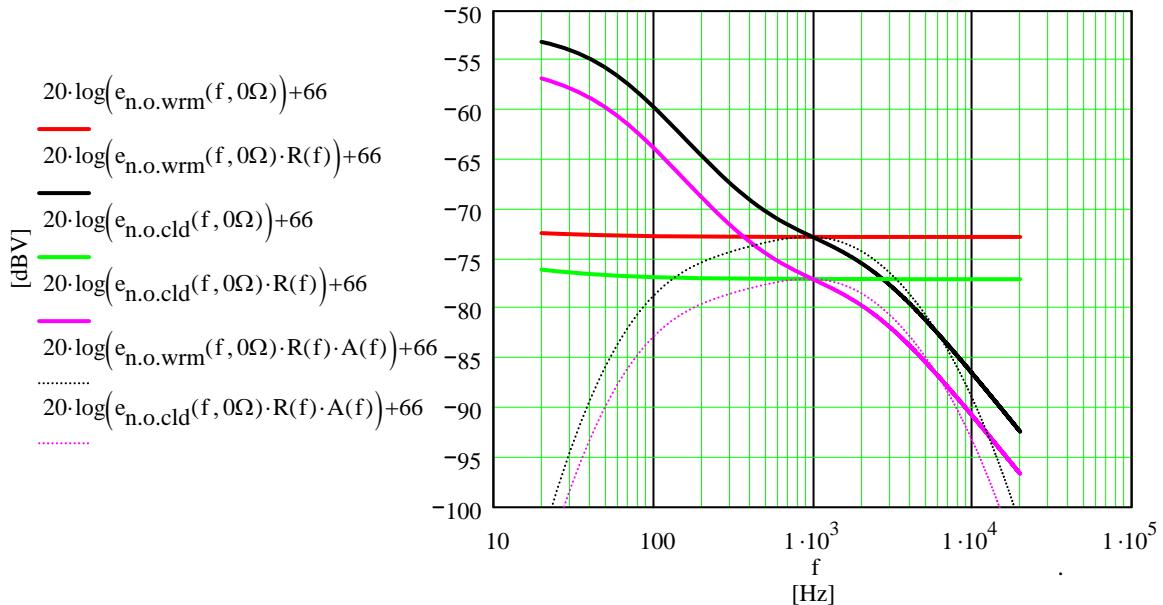
12. Noise of the transformer with $R_0 = 0\Omega$ and after special treatments : $f := 20\text{Hz}, 25\text{Hz}..20\text{kH}\zeta$ 

Fig. 12 Curves of the transformer noise after special treatments

Worsening = Delta red minus green at 1 kHz:

$$W_e(f, R_0) := 20 \cdot \log \left(\frac{e_{n.o.wrm}(f, R_0)}{e_{n.o.cld}(f, R_0)} \right)$$

$$W_e(h, 0\Omega) = 4.239 \quad [\text{dB}]$$