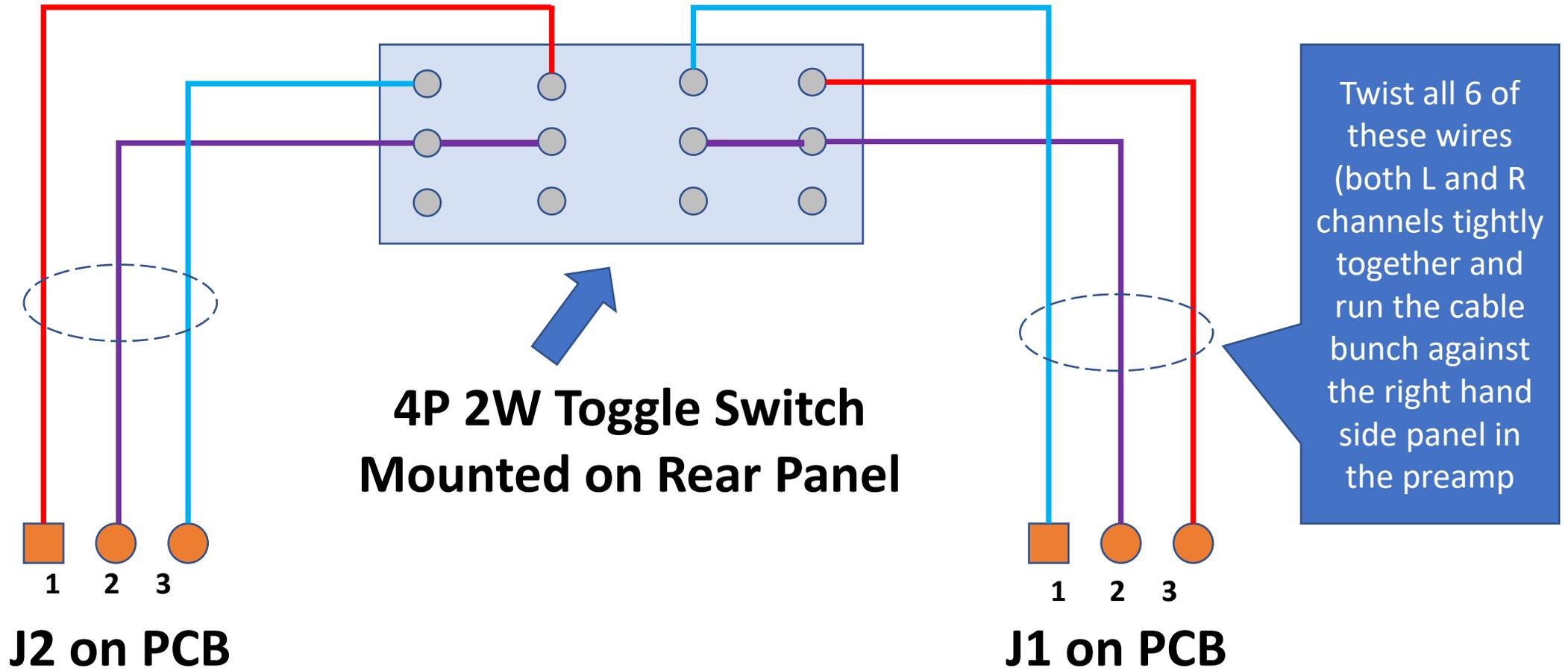
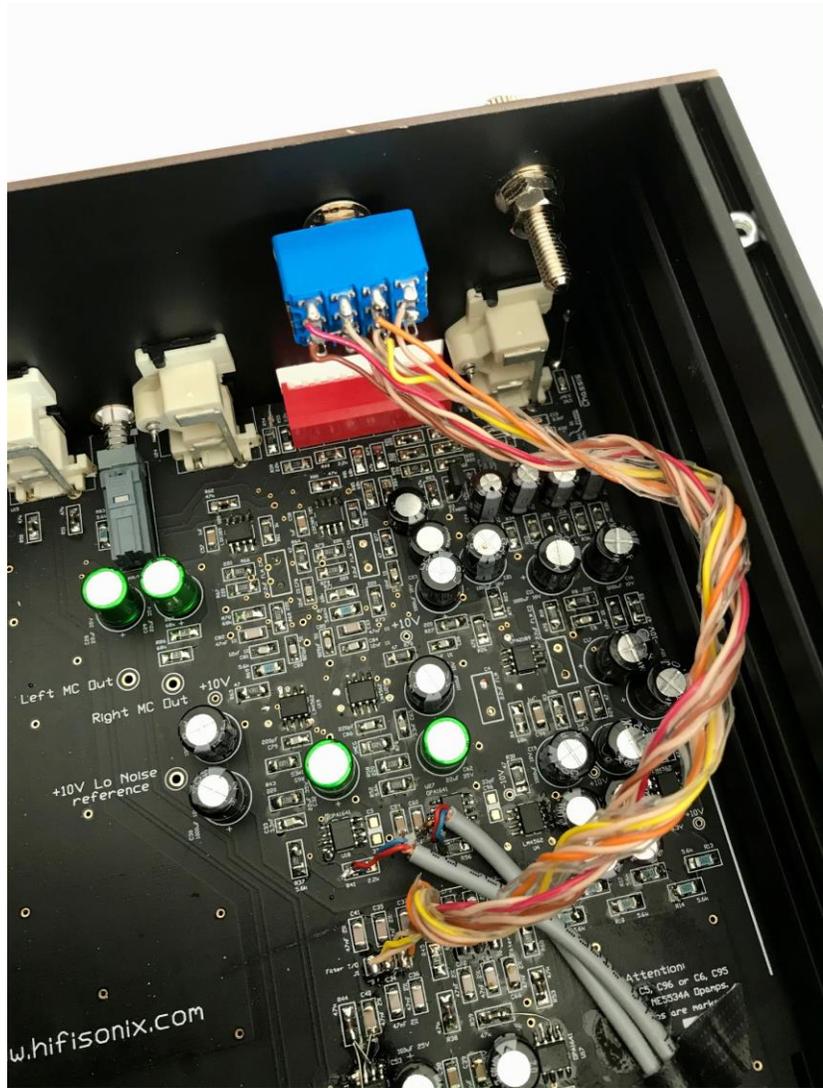


Filter T/O Switch Wiring On The X-altra MC/MM Phono EQ





Here is a picture of my first build (I did 2 builds). For the wires between the switch and the PCB, I used ribbon cable. This wiring is probably suboptimal and should have been twisted a bit more and run closer to the edge of the RHS panel to reduce to opportunity for noise pickup.

Location Of J1 And J2 In The Circuit Diagram

