

# Frequency Tunable Analog Filters: Application to a Linkwitz-Riley Crossover

Numerical filters provide the ability to tune the cut-off frequency, but the anti-aliasing filter must be frequency tunable as well. Though switched capacitors filters allow that, one may prefer a pure analog filter due to noise, distortion or subjective issues. This section presents a method to easily and systematically perform cut-off frequency tuning on any kind of analog filter. A popular LR4 crossover filter using this method will be described.

The method presented here consists of a double approximation. The first approximation is the commonly applied approximation of known analog filters with a numerical system: the following approximation of the  $j\omega$  operator is applied to synthesize the numerical filter:

$$j\omega \approx \frac{2}{T_e} \times \frac{1-z^{-1}}{1+z^{-1}} \tag{1}$$

This approximation turns out to be satisfying if  $F_c \ll F_e$ .

The second approximation consists of approximating the numerical filter with an analog filter. One may approximate pure delays with analog first-order all-pass structures:

$$z^{-1} = e^{-j\omega T_e} \approx \frac{1 - j\omega \times \frac{T_e}{2}}{1 + j\omega \times \frac{T_e}{2}} \tag{2}$$

Combining the approximations from 1 and 2 results in an exact approximation of  $j\omega$ :

$$j\omega \approx \frac{2}{T_e} \times \frac{1-z^{-1}}{1+z^{-1}} \approx \frac{2}{T_e} \times \frac{1 - \frac{1 - j\omega \times \frac{T_e}{2}}{1 + j\omega \times \frac{T_e}{2}}}{1 + \frac{1 - j\omega \times \frac{T_e}{2}}{1 + j\omega \times \frac{T_e}{2}}} = \frac{2}{T_e} \times \frac{1 + j\omega \times \frac{T_e}{2} - 1 + j\omega \times \frac{T_e}{2}}{1 + j\omega \times \frac{T_e}{2} + 1 - j\omega \times \frac{T_e}{2}} = \frac{2}{T_e} \times j\omega \times \frac{T_e}{2} = j\omega \tag{3}$$

Approximation [1] is a mathematical approximation.

Approximation [2] may be achieved in practice with a simple circuit (**Figure A**):

$$\underline{T}(j\omega) = \frac{1 - j\omega \times \frac{T_e}{2}}{1 + j\omega \times \frac{T_e}{2}} = e^{-2 \times \text{arctg}\left(\frac{\omega T_e}{2}\right)}$$

So, we have  $\frac{T_e}{2} = RC$  and R, C should be the same for all occurrence of this circuit.

If you apply this method of complementary approximations, you can get frequency cut-off tuning by changing the identical resistors R of all the necessary first order all-pass structures, and this can be achieved with numerically controlled analog potentiometers or switched capacitors.

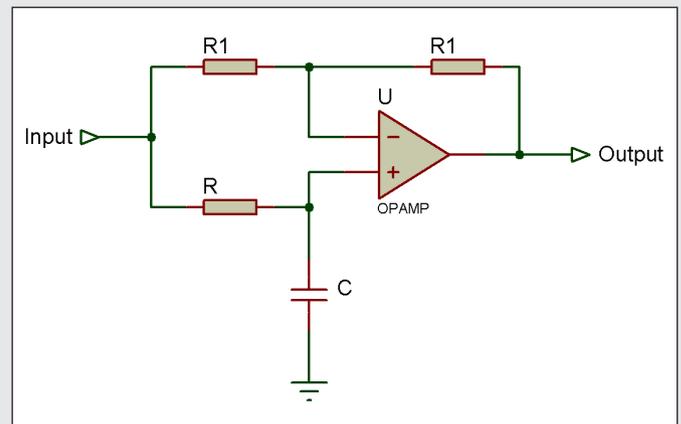


Figure A: A pure delay first-order approximate.

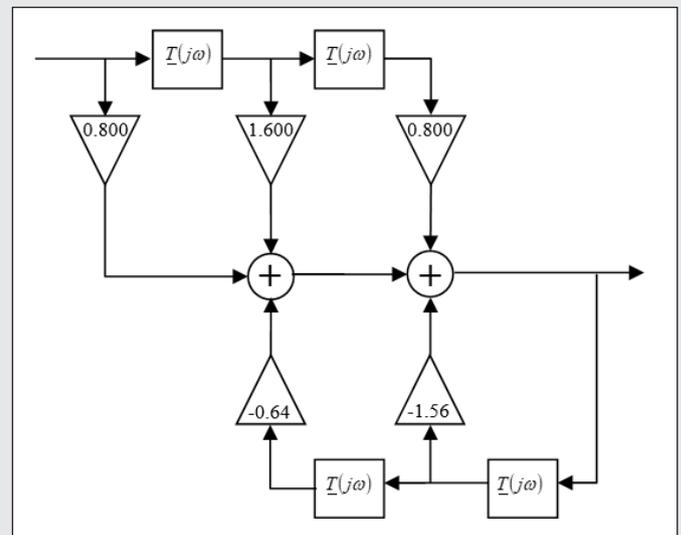


Figure B: A structure for a second-order Butterworth low-pass filter.

Let's take the example of the second-order Butterworth low-pass:

$$\underline{H}(j\omega) = \frac{1}{1 + 2m \frac{j\omega}{\omega_0} + \left(\frac{j\omega}{\omega_0}\right)^2} \approx \frac{1}{1 + 2m \times \frac{2}{\omega_0 T_e} \times \frac{1-z^{-1}}{1+z^{-1}} + \left(\frac{2}{\omega_0 T_e} \times \frac{1-z^{-1}}{1+z^{-1}}\right)^2}$$

with:

$$2m = \sqrt{2} \quad (4)$$

Choose:

$\frac{T_e}{2} = T_0 = RC$ . This is not a good choice for a numerical filter, but it is suitable for our method, where phase rotation of the pseudo-delays is limited to  $\pi$ .

The numerical approximation leads to:

$$\underline{H}(z) \approx \frac{(1+z^{-1})^2}{(1+z^{-1})^2 + \frac{m}{\pi} \times (1-z^{-1}) \times (1+z^{-1}) + \left(\frac{1}{2\pi}\right)^2 \times (1-z^{-1})^2}$$

$$\underline{H}(z) \approx \frac{1 + 2 \times z^{-1} + z^{-2}}{\left(1 + \frac{m}{\pi} + \frac{1}{4\pi^2}\right) + \left(2 - \frac{1}{2\pi^2}\right) \times z^{-1} + \left(1 - \frac{m}{\pi} + \frac{1}{2\pi^2}\right) \times z^{-2}}$$

Then:

$$\left(1 + \frac{m}{\pi} + \frac{1}{4\pi^2}\right) \times S_n + \left(2 - \frac{1}{2\pi^2}\right) \times S_{n-1} + \left(1 - \frac{m}{\pi} + \frac{1}{4\pi^2}\right) \times S_{n-2} = E_n + 2 \times E_{n-1} + E_{n-2}$$

$$S_n = -b_1 \times S_{n-1} - b_2 \times S_{n-2} + a_0 \times E_n + a_1 \times E_{n-1} + a_2 \times E_{n-2}$$

$$\begin{cases} a_0 = \frac{4\pi^2}{(4\pi^2 + 4m\pi + 1)} \approx 0.800 \\ a_1 = \frac{8\pi^2}{(4\pi^2 + 4m\pi + 1)} \approx 1.600 \\ a_2 = \frac{4\pi^2}{(4\pi^2 + 4m\pi + 1)} \approx 0.800 \\ b_1 = \frac{(8\pi^2 - 2)}{(4\pi^2 + 4m\pi + 1)} \approx 1.560 \\ b_2 = \frac{(4\pi^2 - 4m\pi + 1)}{(4\pi^2 + 4m\pi + 1)} \approx 0.640 \end{cases}$$

The corresponding filter is shown in **Figure B**.

Other implementation methods may be used, the important issue being how the filter will behave with respect to components precision.

If you now double the structure of Figure B you get a cut-off frequency-tunable fourth-order Linkwitz-Riley low-pass!

